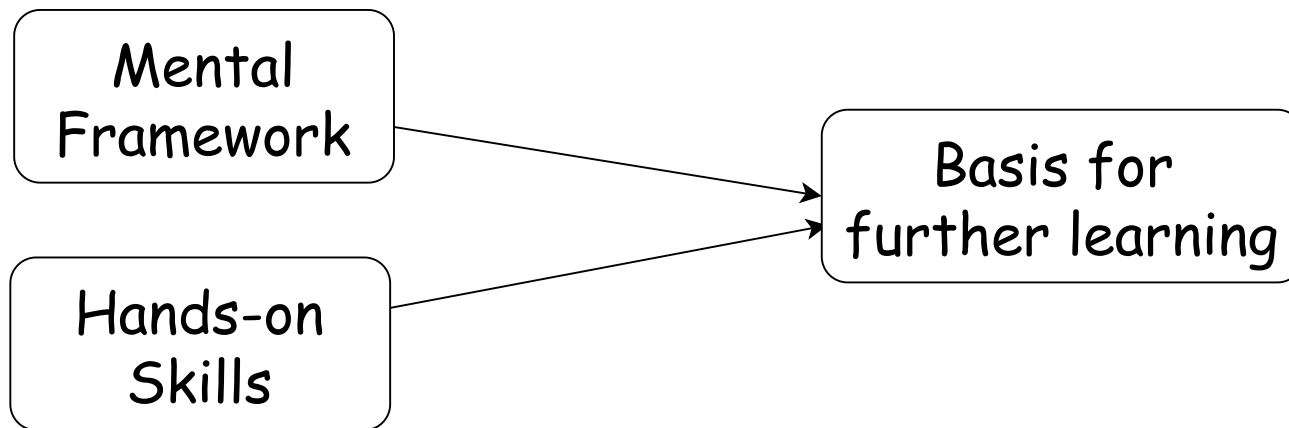


Modular Electronics



The mental framework is vocabulary + concepts.

The main concept is a circuit.

The skills are : using tools, using components and troubleshooting.

Hardware Tools

Power Supply

Digital Voltmeter (DVM)

Solderless Breadboard

Wire strippers

Test cables: banana, alligator, grabber, BNC

Soldering Iron

Oscilloscope

Components

Wire

Resistor

LED

Switch

Potentiometer

Integrated circuits:

Microcontroller (Feather RP2040)

Digital Potentiometer (DS3502)

Input/Output expander (MCP23008)

Components - the bigger picture

Passive

Resistor

Capacitor

Inductor

Active

Diode

Light emitting diode

Transistor

Integrated circuit

CPU

Microcontroller

Operational Amplifier

Comparator, Flip-Flop, etc. etc.

Circuits

Open circuit

Short circuit

Single resistor

Voltage divider

LED with current limiting resistor

RP2040 with USB power and comm link


Pullup resistor

RP2040 OUTPUT pin driving external LED

RP2040 OUTPUT pin driving INPUT pin

Switch driving RP2040 INPUT pin


Resistor

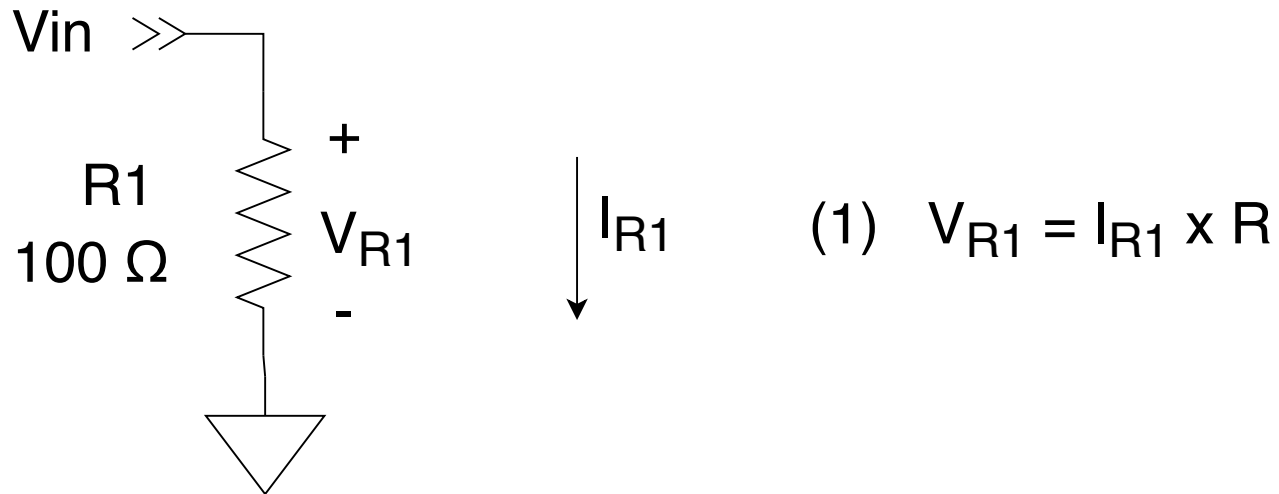

Draw, then build the circuit.

Discussion and demos:
wire, wire stripping,
Power Supply, cables,
solderless breadboard,
Digital Voltmeter

Resistors (voltage divider)

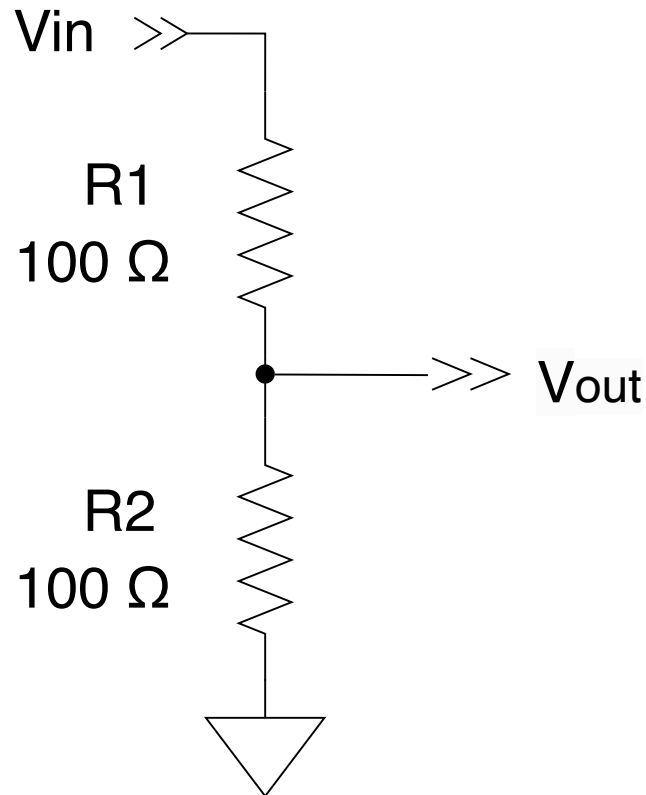

$$R_{equivalent} = R_{series} = R_1 + R_2$$

$$(2) \quad I = I_{R1} = I_{R2} \quad (!!!)$$

$$I = V_{in} / R_{series}$$

$$V_{R1} = I \times R_1$$

$$V_{R2} = I \times R_2$$

$$(3) \quad V_{R1} + V_{R2} = V_{in} \quad (!!!)$$

$$V_{out} = V_{in} - V_{R1}$$

Draw, build and test the circuit.


Discussion and demos:
Safety, Troubleshooting
Circuit Analysis

Resistors + switch


Draw, build and test the circuit, maybe with different R values.

Discussion:

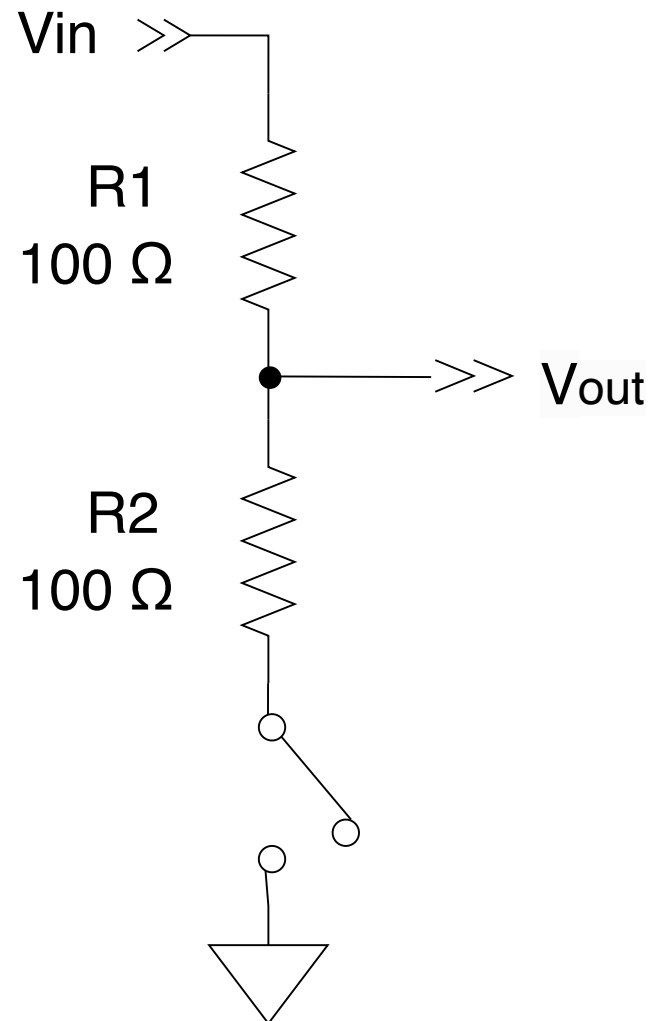Buzzing out your switch.
How does the voltage change when you close the switch?



Resistor + switch + diode

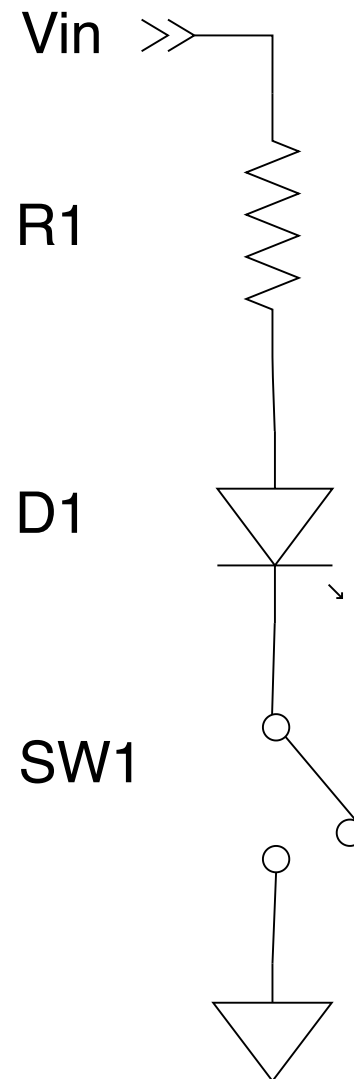

$D1$ turns on when the voltage across it is greater than $\sim 2V$.

$R1$ limits the current through $D1$.

Reference: Analysis Tools

1. Voltage = Current x Resistance (Ohm's Law)
2. Resistive Power Loss = Voltage x Current
3. Series equivalent resistance: $R_{equiv} = R1 + R2 + \dots$
4. Parallel equivalent resistance: $1/R_{equiv} = 1/R1 + 1/R2 + \dots$
5. Current is the same through components in series
6. Voltage is the same across elements in parallel
7. Voltage drops in a series path to ground add up to the voltage at the beginning of the path (Kirchoff's Voltage Law)
8. Currents in parallel paths add up to the current at their common input point (Kirchoff's Current Law)